

**Instructions to the Students:**

1. All the questions are compulsory.
2. Use of non-programmable scientific calculators is allowed.
3. Assume suitable data wherever necessary and mention it clearly.

Marks

**Q.1 Solve Any Two of the following.**

- A) Explain the various operations of regions of a transistor in CE configuration on its output characteristics. **06**
- B) What are different methods of transistor biasing? Explain any one in detail. **06**
- C) The h parameters of a transistor used in a single stage amplifier circuit are  $h_{ic} = 1100$ ,  $h_{rc} = 1$ ,  $h_{fc} = -51$ ,  $h_{oc} = 25\mu A$ . Determine the amplifier parameters for CC configuration when  $R_s = R_L = 10 k\Omega$ . **06**

**Q.2 Solve Any Two of the following.**

- A) What are various characteristics of an ideal Op-Amp? Discuss in details. **06**
- B) Draw the block diagram of an Op-amp and explain the purpose of using each block. **06**
- C) Explain Op-Amp as a differentiator with neat circuit diagram and necessary equations. **06**

**Q.3 Solve Any Two of the following.**

- A) Convert the following numbers: **06**
- a)  $(1101101.101)_2 = ( \quad ? \quad )_{10}$
  - b)  $(126.75)_{10} = ( \quad ? \quad )_8$
  - c)  $(375.75)_{10} = ( \quad ? \quad )_{16}$
- B) Solve the following arithmetic operations **06**
- a) Subtract  $(15)_{10}$  from  $(10)_{10}$  using 2's complement method of binary subtraction.
  - b) Subtract  $(14)_{10}$  from  $(18)_{10}$  using 1's complement method of binary subtraction.
- C) Explain all logic gates with their symbols, output expression and truth table. **06**

**Q.4 Solve Any Two of the following.**

- A) Explain TTL NAND gate circuit (Totem Pole Arrangement) with the help of circuit diagram. **06**
- B) What is meant by MOS logic family? Explain working of NAND gate by NMOS logic. **06**
- C) Explain J-K flip-flop with circuit diagram and truth table. **06**

**Q.5 Solve Any Two of the following.**

- A) Reduce the expression for  $f(A, B, C, D) = \sum_m (0,1,2,3,5,7,8,9,11,14)$  using K-map. **06**
- B) Explain half adder circuit with the truth table. **06**
- C) Reduce the expression for  $f(A, B, C, D) = \pi M (2,3,4,5,6,7,8,11,12)$  **06**